



8-Bit Microprocessor

Designed by/

- **Khaled Gamal**
- **Ahmed Fayad**

Table of Contents

Overview.....	2
Architecture components	2
1- Program Counter:	2
2- Instruction Memory:.....	3
3- ALU (Arithmetic Logic Unit.....	5
4- Control Unit:.....	6
5- Mux0:	8
6- Mux1:	9
7- Sign extender:	10
Top Module	11
Testbench	15
• Code	15
Schematic	16
Simulation output	16

Overview

This project implements a simplified 8-bit microprocessor using VHDL, designed with a modular architecture suitable for simulation-based verification. The microprocessor supports a basic instruction set architecture (ISA) with operations such as ADD, SUB, AND, and ADDI, and is structured around a classic single-cycle Datapath.

Architecture components

The processor is composed of the following key modules:

1- Program Counter:

The Program Counter is a critical component in the microprocessor design that determines the sequence of instruction execution. It provides the address of the next instruction to be fetched from the instruction memory.

➤ Functionality:

- The PC is implemented as a 3-bit counter (allowing a total of 8 instruction addresses: 0 to 7).
- It increments its value by 1 on every **falling edge** of the clock.
- The current value of the counter is output as next instruction, which is used as the address input to the instruction memory.

▪ Code

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Program_counter is
    port (
        clk      : in std_logic;
        next_instruction : out STD_LOGIC_VECTOR(2 downto 0)
    );
end entity Program_counter;

architecture rtl of Program_counter is

    --Storing the value to be displayed in the output
    signal current_signal : std_logic_vector(2 downto 0) := "000";

begin
    process (clk)
    begin
        if falling_edge(clk) then
            current_signal <= STD_LOGIC_VECTOR(unsigned(current_signal) +
TO_UNSIGNED(1,3));
        end if;
    end process;


    next_instruction <= current_signal;
end architecture;

```

2-Instruction Memory:

This module simulates a small read-only memory (ROM) that stores 8 predefined 8-bit instructions. Each instruction is decoded into four 2-bit segments:

 - **op**: ALU operation code (bit 7 & 6)
- **rs_addr**: source register (A) (bit 5 & 4)
- **rt_addr**: target register (B) (bit 3 & 2)
- **rd_addr**: destination register (bit 1 & 0)



Behavior:

- instr_addr (3-bit input) selects one of the 8 instructions.
- The selected instruction is split into segments and routed to the respective outputs (op, rs_addr, etc.).

■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Instruction_memory is
    port (
        instr_addr : in std_logic_vector(2 downto 0);
        op : out std_logic_vector(1 downto 0);
        rs_addr : out std_logic_vector(1 downto 0);           --Address of source register
        rt_addr : out std_logic_vector(1 downto 0);           --Address of target register
        rd_addr : out std_logic_vector(1 downto 0);           --Address of destination register
    );
end entity Instruction_memory;


architecture rtl of Instruction_memory is
    --Construction of the memory which is 8-bit long and each row is 8-bit wide
    type instruction_set is array (0 to 7) of std_logic_vector(7 downto 0);
    constant instr : instruction_set := (
        "01000010",
        "11010101",
        "11101011",
        "01000111",
        "10101100",
        "00000000",
        "00000000",
        "00000000"
    );
begin
    op <= instr (to_integer(unsigned(instr_addr))) (7 downto 6);
    rs_addr <= instr (to_integer(unsigned(instr_addr))) (5 downto 4);
    rt_addr <= instr (to_integer(unsigned(instr_addr))) (3 downto 2);
    rd_addr <= instr (to_integer(unsigned(instr_addr))) (1 downto 0);
end architecture;
```

3- ALU (Arithmetic Logic Unit)

Performs basic arithmetic/logic operations between two 8-bit inputs (rs and rt) based on the 2-bit op code.

Supported Operations:

 - "00": AND
- "01": Addition
- "10": Subtraction
- "11": Addition with special behavior (used in addi-like instruction)



Output:

- Result is assigned to rd.

■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;      --unsigned variables

entity ALU is
    port (
        op : in std_logic_vector(1 downto 0);
        rs , rt : in std_logic_vector(7 downto 0);
        rd : out std_logic_vector(7 downto 0)
    );
end entity ALU;

architecture rtl of ALU is
    signal result : std_logic_vector(7 downto 0);
begin

    process (op , rs , rt)
    begin
        if (op = "00") then      --AND operation
            result <= rs and rt;
        elsif (op = "01") then  --Addition operation
            result <= rs + rt ;
        elsif (op = "10") then  --Subtraction operation
            result <= rs - rt ;
        end if;
    end process;
end architecture;
```

```

        elsif (op = "11") then    --Addition operation 2 and this operation is done using the
control unit
            result <= rs + rt ;    -- Adding A with the address of the destination register
(8-bit + 2-bit) and the result will be saved in register2
        end if;
    end process;

    --Assigning the result to the output
    rd <= result;

end architecture;

```

4- Control Unit:

Controls the datapath behavior based on the opcode of the current instruction.

Inputs:


- instr: 2-bit ALU opcode.

Outputs:

- alu_op: opcode passed to the ALU.
- alu_src: select signal for mux1 (selects ALU input operand: reg2 address vs destination register address).
- reg_dst: select signal for mux0 (selects destination register: rd vs register2 value).

Behavior:

 - For normal ops ("00", "01", "10"), both muxes are set to default.
- For special op "11" (addi), muxes are reconfigured.



■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Control_unit is
    port (
        instr : in STD_LOGIC_VECTOR (1 downto 0);    --input to choose which operation
        alu_op : out STD_LOGIC_VECTOR (1 downto 0);    --same opcode will be output here but
        the difference is in the muxs
        alu_src : out std_logic;                        --selection line of mux1
        reg_dst : out std_logic                        --selection line of mux0
    );
end entity Control_unit;

architecture rtl of Control_unit is

begin
    --assinging the output to be the same as the input which will be the to ALU opcode
    with instr select
        alu_op <= "00" when "00",        --AND
                  "01" when "01",        --Add
                  "10" when "10",        --Sub
                  "11" when others;      --Addi

    --Controlling the mux0 selection line
    with instr select
        reg_dst <= '1' when "11",        --Addi
                  '0' when others;

    --Controlling the mux1 selection line
    with instr select
        alu_src <= '1' when "11",        --Addi
                  '0' when others;

end architecture rtl;
```


5- Mux0:


Selects the destination register address.

Inputs:

- a: address of register2
- b: default rd register address
- sel: selector (1 for a, 0 for b)

Output:

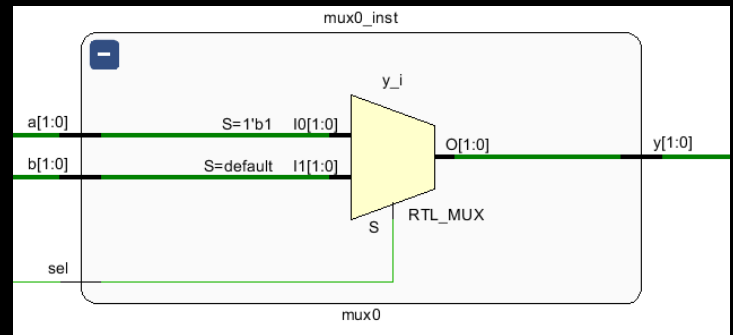- y: selected register address and pass it to the registers file



■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

--This mux chooses the address of which register the data will be saved inside
entity mux0 is
    port (
        a : in STD_LOGIC_VECTOR (1 downto 0);           --address of reg2
        b : in STD_LOGIC_VECTOR (1 downto 0);           --default destination address
        sel : in std_logic;
        y : out STD_LOGIC_VECTOR (1 downto 0)           --destination address
    );
end entity mux0;

architecture behavioral of mux0 is
begin
    process (sel , a , b)
    begin
        if (sel = '1') then    --This operation is done in case of opcode = 11
            y <= a;
        else
            y <= b;            -- default operations will be done while opcode = 00 or 01 or 10
        end if;
    end process;
end architecture behavioral;
```

6- Mux1:


Chooses the second operand to send to the ALU.

Inputs:

- a: value from register2
- b: sign-extended constant (from rd_addr)
- sel: selector (1 for b, 0 for a)

Output:

- y: ALU operand

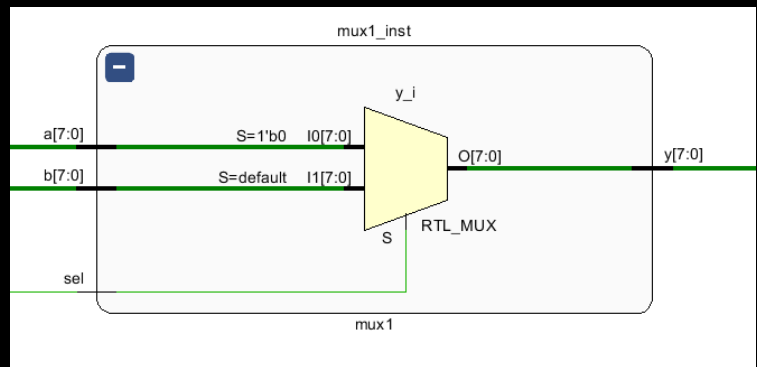


■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

--This mux will choose the value of the data to be added together
entity mux1 is
    port (
        a : in STD_LOGIC_VECTOR (7 downto 0);           --default data
        b : in STD_LOGIC_VECTOR (7 downto 0);           --constant data
        sel : in std_logic;
        y : out STD_LOGIC_VECTOR (7 downto 0)           --output data
    );
end entity mux1;
architecture behavioral of mux1 is
begin
    process (sel , a , b)
    begin
        if (sel = '0') then    --default operations (opcode = 00 or 01 or 10)
            y <= a;
        else
            y <= b;            --when opcode = 11
        end if;
    end process;
end architecture behavioral;
```

7- Sign extender:

 Extends a 2-bit value (rd_addr) to 8 bits by padding 6 leading zeros.



Use Case:

Used to convert destination register address into a value that can be added to a register (for immediate-like instructions such as addi).

■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity sign_extend is
    port (
        data_in : in STD_LOGIC_VECTOR (1 downto 0);
        data_out : out STD_LOGIC_VECTOR (7 downto 0)
    );
end entity sign_extend;

architecture rtl of sign_extend is
begin
    data_out <= "000000" & data_in;
end architecture rtl;
```

Top Module

■ Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity CPU_top is
    port (
        clk : in std_logic;
        value : out std_logic_vector(7 downto 0)
    );
end entity CPU_top;

architecture rtl of CPU_top is

    --Components declaration
    component Program_counter is
        port (
            clk : in std_logic;
            next_instruction : out STD_LOGIC_VECTOR(2 downto 0)

        );
    end component Program_counter;

    component Instruction_memory is
        port (
            instr_addr : in std_logic_vector(2 downto 0);
            op : out std_logic_vector(1 downto 0);
            rs_addr : out std_logic_vector(1 downto 0);
            rt_addr : out std_logic_vector(1 downto 0);
            rd_addr : out std_logic_vector(1 downto 0)
        );
    end component Instruction_memory;

    component Registers_file is
        port (
            clk : in std_logic;
            rs_addr : in std_logic_vector(1 downto 0);
            rt_addr : in std_logic_vector(1 downto 0);
            rd_addr : in std_logic_vector(1 downto 0);
            wr_data : in std_logic_vector(7 downto 0);
            rs : out std_logic_vector(7 downto 0);
            rt : out std_logic_vector(7 downto 0)
        );
    end component Registers_file;
```

```

component ALU is
    port (
        op : in std_logic_vector(1 downto 0);
        rs , rt : in std_logic_vector(7 downto 0);
        rd : out std_logic_vector(7 downto 0)
    );
end component ALU;

```

```

component Control_unit is
    port (
        instr : in STD_LOGIC_VECTOR (1 downto 0);
        alu_op : out STD_LOGIC_VECTOR (1 downto 0);
        alu_src : out std_logic;
        reg_dst : out std_logic
    );
end component Control_unit;

```

```

component mux0 is
    port (
        a : in STD_LOGIC_VECTOR (1 downto 0);
        b : in STD_LOGIC_VECTOR (1 downto 0);
        sel : in std_logic;
        y : out STD_LOGIC_VECTOR (1 downto 0)
    );
end component mux0;

```

```

component mux1 is
    port (
        a : in STD_LOGIC_VECTOR (7 downto 0);
        b : in STD_LOGIC_VECTOR (7 downto 0);
        sel : in std_logic;
        y : out STD_LOGIC_VECTOR (7 downto 0)
    );
end component mux1;

```

```

component sign_extend is
    port (
        data_in : in STD_LOGIC_VECTOR (1 downto 0);
        data_out : out STD_LOGIC_VECTOR (7 downto 0)
    );
end component sign_extend;

```

--Signals declaration

```

signal opcode_sig : std_logic_vector(1 downto 0);
signal rs_sig , rt_sig : std_logic_vector(7 downto 0);
signal instr_sig : std_logic_vector(1 downto 0);

```

```

signal alu_dst_sig, alu_src_sig : STD_LOGIC;
signal rt_addr_sig , rd_addr_sig : std_logic_vector(1 downto 0);
signal rt_val , sign_ext_out: std_logic_vector(7 downto 0);
signal mux0_out , rs_addr_sig : std_logic_vector(1 downto 0);
signal instr_addr_sig : std_logic_vector(2 downto 0);
signal out_val : std_logic_vector(7 downto 0);

```

```
begin
```

```
    value <= out_val;
```

```
--Components instantiation
```

```
    ALU_inst:
```

```
    ALU port map(
```

```
        op => opcode_sig,
```

```
        rs => rs_sig,
```

```
        rt => rt_sig,
```

```
        rd => out_val
```

```
    );
```

```
    Control_unit_inst: Control_unit
```

```
    port map(
```

```
        instr => instr_sig,
```

```
        alu_op => opcode_sig,
```

```
        alu_src => alu_src_sig,
```

```
        reg_dst => alu_dst_sig
```

```
    );
```

```
    Instruction_memory_inst: Instruction_memory
```

```
    port map(
```

```
        instr_addr => instr_addr_sig,
```

```
        op => instr_sig,
```

```
        rs_addr => rs_addr_sig,
```

```
        rt_addr => rt_addr_sig,
```

```
        rd_addr => rd_addr_sig
```

```
    );
```

```
    mux0_inst: mux0
```

```
    port map(
```

```
        a => rt_addr_sig,
```

```
        b => rd_addr_sig,
```

```
        sel => alu_dst_sig,
```

```
        y => mux0_out
```

```
    );
```

```
    mux1_inst: mux1
```

```
    port map(
```

```
        a => rt_val,
```

```
        b => sign_ext_out,
```

```

        sel => alu_src_sig,
        y => rt_sig
    );

Program_counter_inst: Program_counter
port map(
    clk => clk,
    next_instruction => instr_addr_sig
);

Registers_file_inst: Registers_file
port map(
    clk => clk,
    rs_addr => rs_addr_sig,
    rt_addr => rt_addr_sig,
    rd_addr => mux0_out,
    wr_data => out_val,
    rs => rs_sig,
    rt => rt_val
);

sign_extend_inst: sign_extend
port map(
    data_in => rd_addr_sig,
    data_out => sign_ext_out
);
end architecture;
```

Testbench

- Code

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity CPU_tb is
end entity CPU_tb;

architecture rtl of CPU_tb is
    component CPU_top is
        port (
            clk : in std_logic;
            value : out std_logic_vector(7 downto 0)
        );
    end component CPU_top;

    signal clk_tb : STD_LOGIC := '0';
    signal value_tb : std_logic_vector(7 downto 0) := "00000000";


begin

    dut:CPU_top
    port map(
        clk => clk_tb,
        value => value_tb
    );

    clk_generation: process
    begin
        while true loop
            wait for 5 ns;
            clk_tb <= not clk_tb;
        end loop;
    end process clk_generation;

    stim_proc: process
    begin
        wait for 200 ns;
        wait;
    end process stim_proc;
end architecture;
```


Schematic

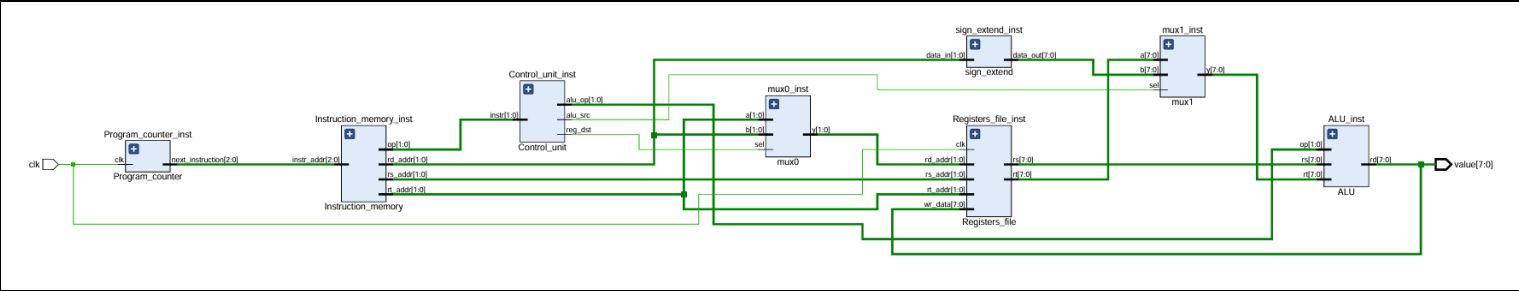

Simulation output

